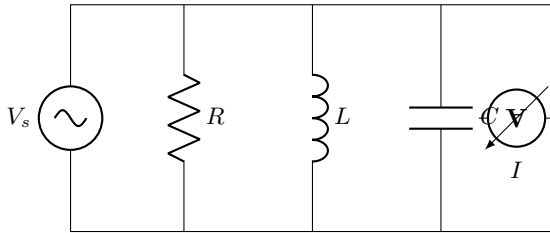


Parallel LCR circuit



At anti-resonance, supply current is minimum and impedance is maximum.